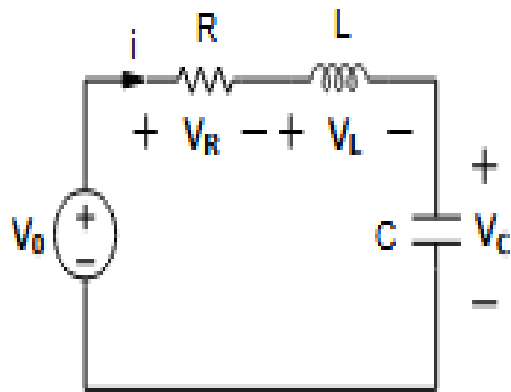


ELECTRICAL CIRCUITS

RLC Circuits with DC Source

Rubina Akter Sathi
Department of ECE
National Institute of Science And Technology

Series RLC circuit:



$$\text{KVL: } V_R + V_L + V_C = V_0 \Rightarrow iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_0$$


Differentiating w. r. t. t , we get,

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i = 0.$$

$$\text{i.e., } \frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0,$$

a second-order ODE with constant coefficients.

Parallel RLC circuit:

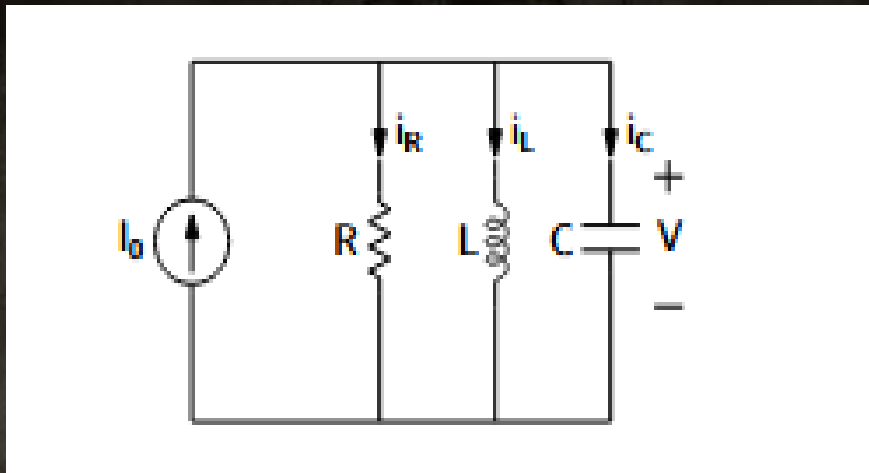

$$\text{KCL: } i_R + i_L + i_C = i_0 \Rightarrow \frac{1}{R} V + \frac{1}{L} \int V dt + C \frac{dV}{dt} = i_0$$


Differentiating w. r. t. t , we get,

$$\frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V + C \frac{d^2V}{dt^2} = 0.$$

$$\text{i.e., } \frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0,$$

a second-order ODE with constant coefficients.

Series/Parallel RLC circuits:

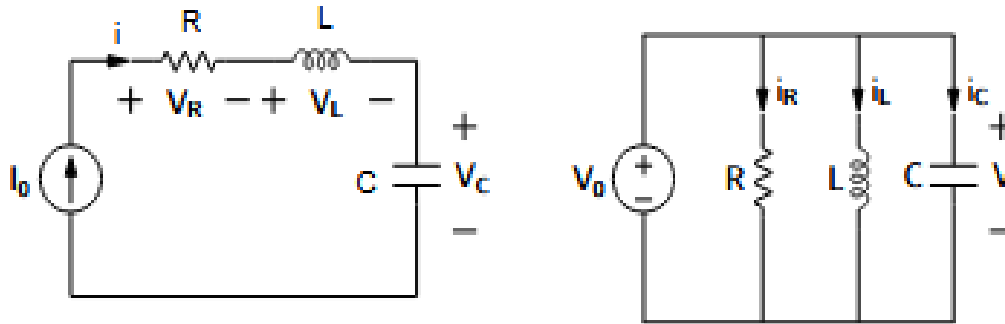

- * A series RLC circuit driven by a constant current source is trivial to analyze. Since the current through each element is known, the voltage can be found in a straightforward manner.

$$V_R = iR, V_L = L \frac{di}{dt}, V_C = \frac{1}{C} \int i dt.$$

- * A parallel RLC circuit driven by a constant voltage source is trivial to analyze. Since the voltage across each element is known, the current can be found in a straightforward manner.

$$i_R = V/R, i_C = C \frac{dV}{dt}, i_L = \frac{1}{L} \int V dt.$$